

Voltage and current in a parallel connection of solar cells

Task and equipment

Information for teachers

Additional Information

The pupils should examine a parallel connection of solar cells by measuring the open circuit voltage, U_{ges} , and the short-circuit current, I_{ges} .

Using a connection in parallel, greater currents can be reached.

Furthermore, the currents I_1 and I_2 at each solar cell will be measured. Using this information and I_{ges} , the relation for the parallel connection of the solar cells can be derived: $I_{ges} = I_1 + I_2$.

The voltage at each solar cell is equal to the open circuit voltage, U_{ges} : $U_{ges} = U_1 = U_2$.

Voltage and current in a parallel connection of solar cells

Task and equipment


Task

What happens when you connect two solar cells in parallel?

Connect two solar cells in parallel and examine the voltage and the current.



Equipment

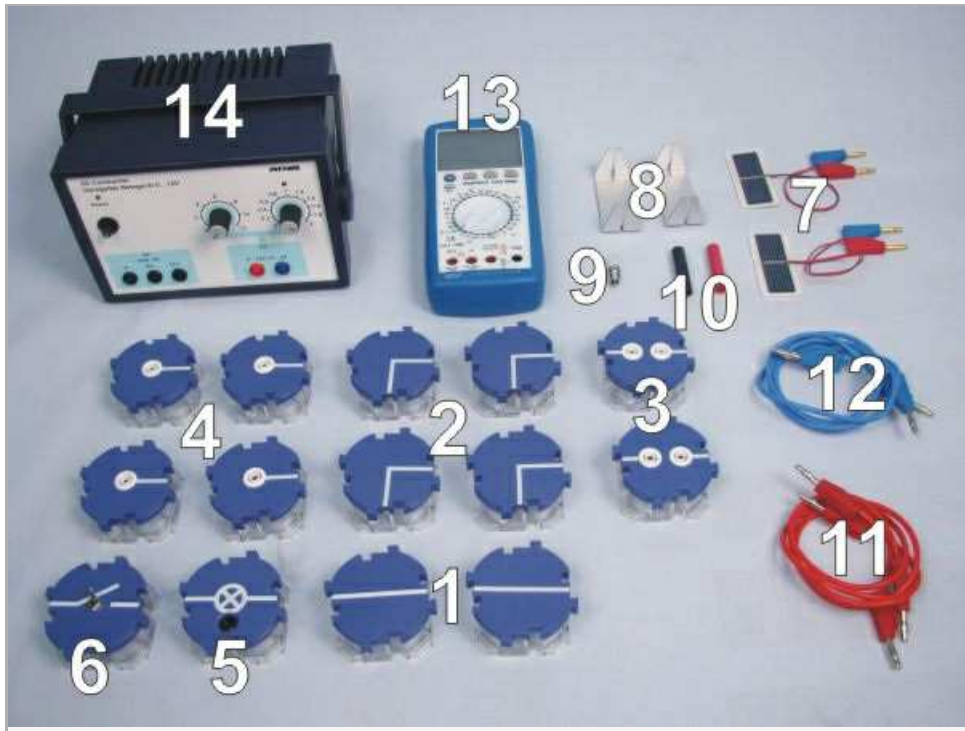

| Position No. | Material | Order No. | Quantity |
|--------------|---|-----------|----------|
| 1 | Straight connector module, SB | 05601-01 | 2 |
| 2 | Angled connector module, SB | 05601-02 | 4 |
| 3 | Interrupted connector module, SB | 05601-04 | 2 |
| 4 | Junction module, SB | 05601-10 | 4 |
| 5 | Socket module for incandescent lamp E10, SB | 05604-00 | 1 |
| 6 | On-off switch module, SB | 05602-01 | 1 |
| 7 | Solar cell 2.5 x5 cm, with plugs | 06752-11 | 2 |
| 8 | Holder for solar cell 2.5 x5 cm, with plugs | 06752-12 | 2 |
| 9 | Filament lamp 6 V/3 W, E10, 10 pcs. | 35673-03 | (1) |
| 10 | Double sockets, 1 pair, red a. black | 07264-00 | 1 |
| 11 | Connecting cord, 32 A, 500 mm, red | 07361-01 | 2 |
| 12 | Connecting cord, 32 A, 500 mm, blue | 07361-04 | 2 |
| 13 | DMM with NiCr-Ni thermo couple | 07122-00 | 1 |
| 14 | PHYWE power supply DC: 0...12 V, 2 A / AC: 6 V, 12 V, 5 A | 13506-93 | 1 |


Set-up and procedure

Set-up

Build the lamp circuit as in Fig. 1. Then prepare the circuit for the solar cells (Fig. 2).



Join both circuits as shown in Fig. 3.

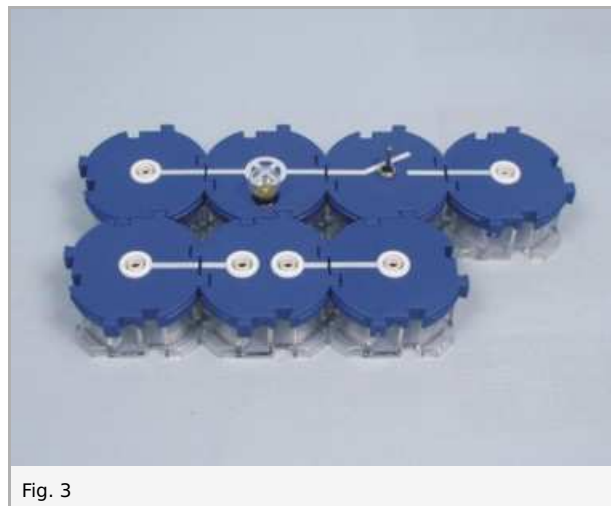

Place each cell in its holder (Fig. 4) and connect them as shown in Fig. 5.

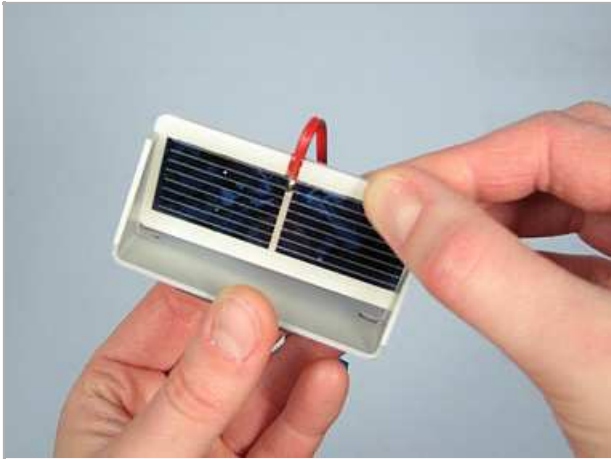


Fig. 4

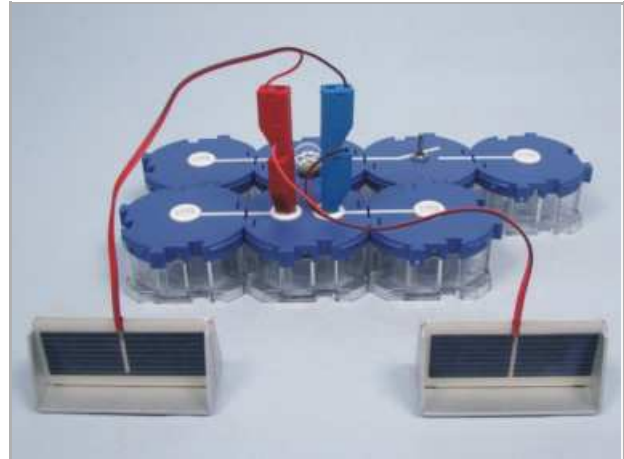


Fig. 5

Place the solar cells next to the bulb at the same distance (Fig. 6).

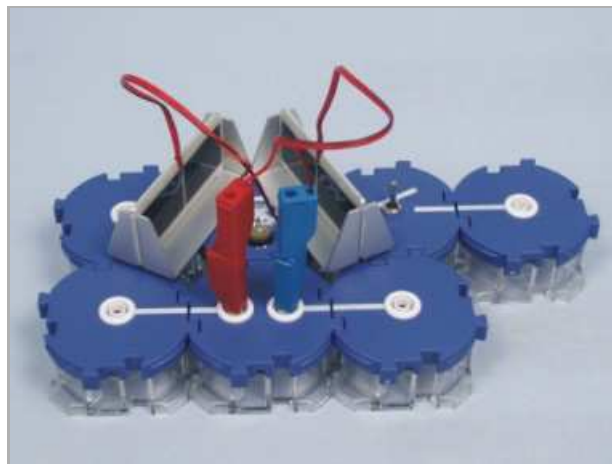


Fig. 6

Procedure

Measuring the voltage

Connect the lamp circuit to the power supply, as shown in Fig. 7.

The power supply is off and the on-off switch in the circuit is open.

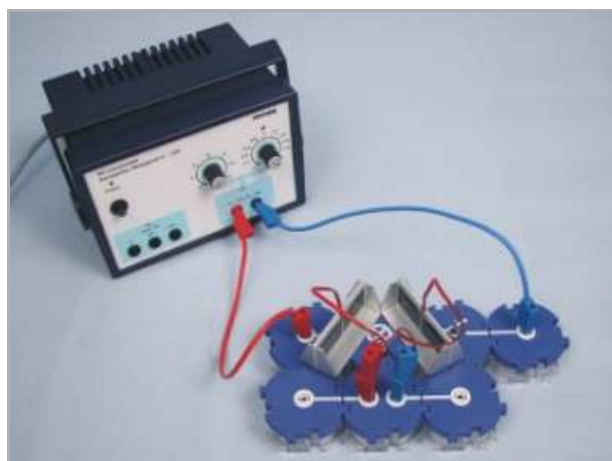


Fig. 7

Student's Sheet

Printed: 13.04.2017 16:47:29 | P9511400

Set the measuring range of the multimeter to 20 V- and connect it to the solar cell circuit (Fig. 8).

Turn on the power supply and set the voltage knob to 6 V.

Close the on-off switch in the circuit and turn on the measurement device.

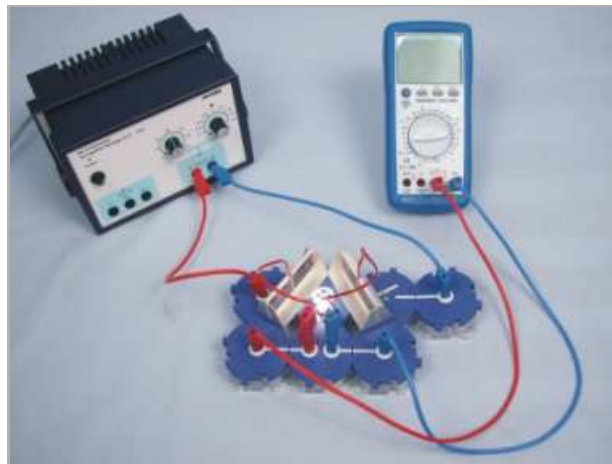


Fig. 8

Read the voltage displayed, U_{ges} , and write it down in Result - Observations in the report.

Measuring the current

Open the on-off switch.

Build a circuit for the solar cells with which you can measure the current (Fig. 9).

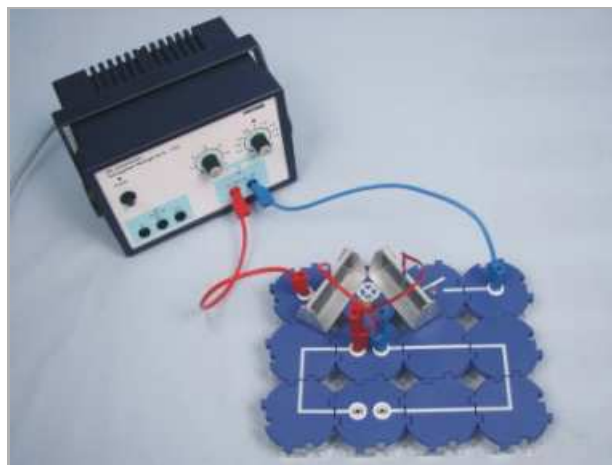


Fig. 9

Set the measuring range of the multimeter to 200 mA- and connect it (Fig. 10).

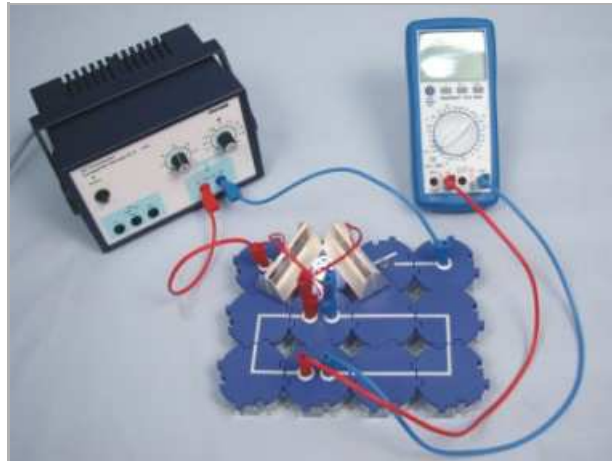


Fig. 10

Close the on-off switch, read the total current, I_{ges} , and write it down in Result - Observations.

Rebuild the circuit so that you can read the current of each cell (Fig. 11).

Close the on-off switch and read the current I_1 at the first cell.

Repeat the measurement for the second cell and read the current I_2 . Record the results in Result - Observations.

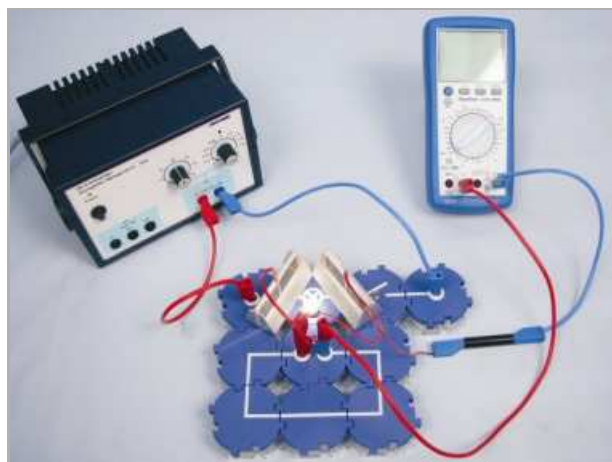


Fig. 11

Report: Voltage and current in a parallel connection of solar cells

Result - Observations

Record your measured values:

$U_{ges} = \dots\dots\dots$ V

$I_{ges} = \dots\dots\dots$ mA

$I_1 = \dots\dots\dots$ mA

$I_2 = \dots\dots\dots$ mA

Evaluation - Question 1

What can be achieved by connecting solar cells in parallel?

.....

.....

.....

.....

Evaluation - Question 2

What is the relation between the total current, I_{ges} , and the current values for the individual cells, I_1 and I_2 , in the case of a connection in parallel?

.....

.....

.....

.....